

## Lab 6 – BJT Common-Emitter Circuit

\* Standard Value Only    !!! Substantial Error (Inconclusive)

Parameter	Formulas See Appendix	Calculated Value Ideal Resistors	Calculated Value Measured Resistors	Measured Value or Calc. from Meas.	Error Ideal Resistors	Error Measured Resistors
$v_{in} = 100 \text{ mV (Pk-Pk)}$				104 mV		4.00%
$f_{in} = 10 \text{ kHz}$				10.03 kHz		0.30%
$V_{CC} = 10 \text{ V}$				10.00 V		0.00%
$V_{EE} = -10 \text{ V}$				-10.00 V		0.00%
$R_F = 10 \text{ k}\Omega$				9.83 k\Omega		1.70%
$R_L = 10 \text{ k}\Omega$				9.86 k\Omega		1.40%
$R_C$	(1)	1 k\Omega		0.98 k\Omega		2.00%
$R_{E1} = 50 \text{ }\Omega$			51 \Omega	50.8 \Omega		0.39%
$R_{E2}$	(18)	918.91 \Omega	910 \Omega	940 \Omega		3.30%
$C_C$	(12)	1.9284 \mu F	*2.2 \mu F			
$C_B$	(10)	3.4600 \mu F	*3.3 \mu F			
$C_E$	(20)	31.998 \mu F	*33 \mu F			
$A_v (\text{V/V}) = -20 \text{ V/V}$	(21)	-15.692 V/V	-15.401 V/V	NA	NA	NA
$A_v (\text{dB}) = 26.02 \text{ dB}$	(22)	23.914 dB	23.751 dB	NA	NA	NA
$g_m$	(2)	385.31 mA/V				
$f_{min} = 100 \text{ Hz}$				NA	NA	NA
$\alpha = \beta / (\beta + 1)$	NA	256/257				
$\beta = 256$						
$V_A = 74.03 \text{ V}$						
$V_T = 25.8519 \text{ mV}$						
$V_C$	(15)	10 V		3.15 V	!!!	!!!
$V_B$	(16)	389.11 mV		-2.40 V	!!!	!!!
$V_E$	(17)	-310.89 mV		-3.05 V	!!!	!!!
$V_B - V_E \approx 0.7 \text{ V}$						
$I_C$	(13)	9.9611 mA		NA	NA	NA
$I_B$	(14)	38.911 \mu A		NA	NA	NA
$I_E = 10 \text{ mA}$				NA	NA	NA
$r_o$	(3)	7.4319 k\Omega				
$r_\pi$	(4)	664.39 \Omega				
$R_{\text{coll.}}$	(5)	150.66 k\Omega	153.53 k\Omega			
$R_{\text{base}}$	(6)	13.514 k\Omega	13.771 k\Omega			
$R_{\text{in,F}}$	(7)	476.19 \Omega				
$R_{\text{out,F}}$	(8)	9.5238 k\Omega				
$R_{C,\text{tot}}$	(11)	825.33 \Omega	825.41 \Omega			
$R_{B,\text{tot}}$	(9)	459.98 \Omega	460.27 \Omega			
$R_{E,\text{tot}}$	(19)	49.739 \Omega	50.605 \Omega			

## Appendix

$$(1) A_v \approx -\frac{R_C}{R_{E1}}$$

$$(2) g_m = \frac{\alpha I_E}{V_T} = \frac{I_C}{V_T}$$

$$(3) r_o = \frac{V_A}{\alpha I_E} = \frac{V_A}{I_C}$$

$$(4) r_\pi = \frac{\beta}{g_m}$$

$$(5) R_{\text{coll.}} = R_{E1} + r_o + g_m r_o R_{E1} \quad (6) R_{\text{base}} = r_\pi + (\beta + 1) R_{E1}$$

$$(7) R_{\text{in,F}} = \frac{R_F}{1 + |A_v|}$$

$$(8) R_{\text{out,F}} = \frac{R_F}{1 + 1/|A_v|}$$

$$(9) R_{B,\text{tot}} = R_{\text{base}} \parallel R_{\text{in,F}}$$

$$(10) C_B = \frac{1}{2\pi f_{\min} R_{B,\text{tot}}}$$

$$(11) R_{C,\text{tot}} = R_C \parallel R_L \parallel R_{\text{coll.}} \parallel R_{\text{out,F}}$$

$$(12) C_C = \frac{1}{2\pi f_{\min} R_{C,\text{tot}}}$$

$$(13) I_C = \alpha I_E$$

$$(14) I_B = I_C / \beta$$

$$(15) V_C = R_C (I_C + I_B)$$

$$(16) V_B = R_F I_B$$

$$(17) V_B - V_E \approx 0.7$$

$$(18) V_E - V_{EE} = (R_{E1} + R_{E2}) I_E$$


$$(19) R_{E,\text{tot}} = \left( R_{E1} + \frac{\alpha}{g_m} \right) \parallel R_{E2}$$

$$(20) C_E = \frac{1}{2\pi f_{\min} R_{E,\text{tot}}}$$


$$(21) A_v (\text{V/V}) = \frac{-g_m R_{C,\text{tot}}}{1 + g_m R_{E1}}$$

$$(22) A_v (\text{dB}) = 20 \log |A_v (\text{V/V})|$$


**CD.1**

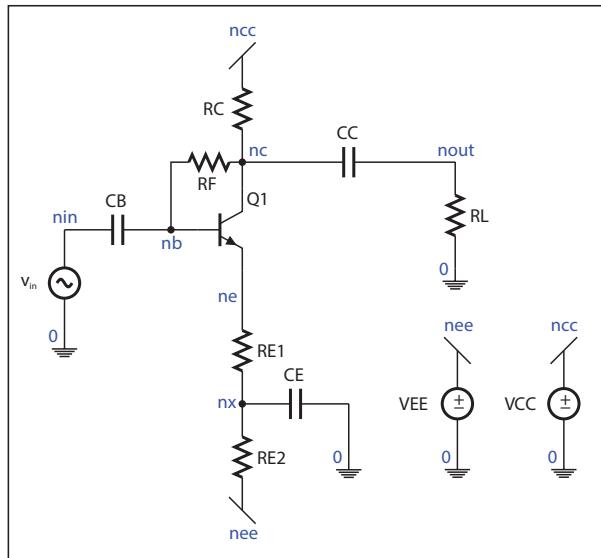

**PL.1**

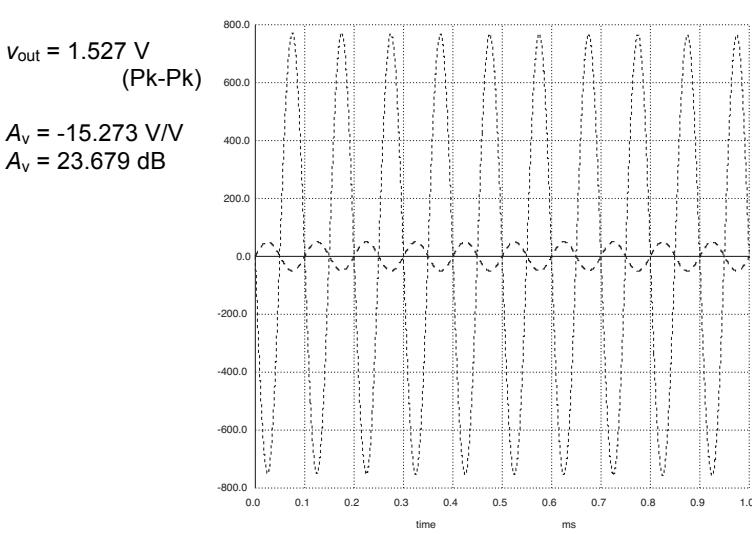


**PL.2**

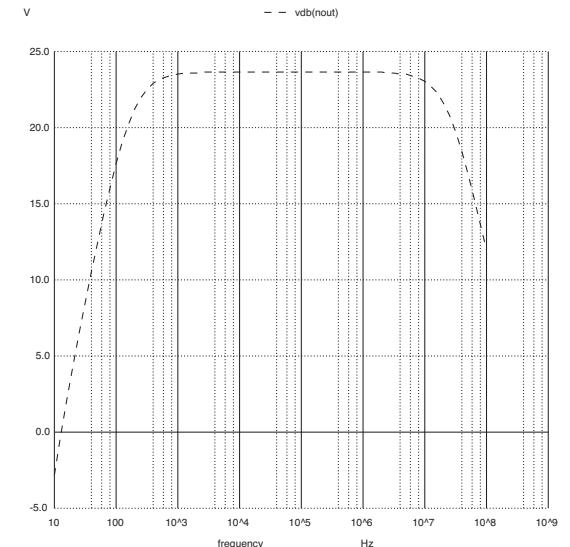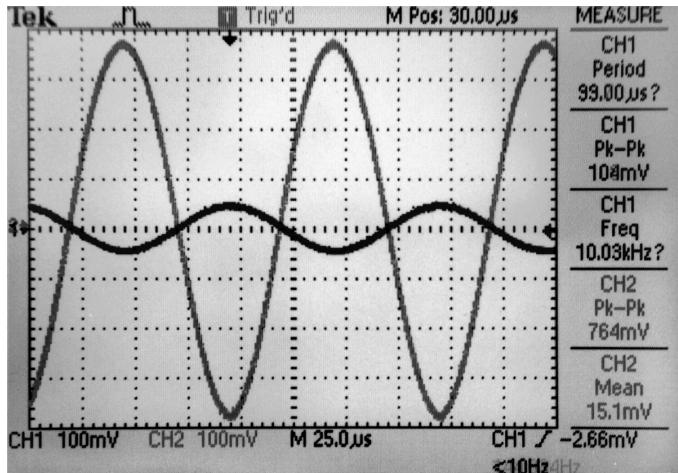

**OP.1**


$$V_{out} = 764 \text{ mV} \quad (\text{Pk-Pk})$$

$$V_{in} (\text{CH1}) \\ V_{out} (\text{CH2})$$

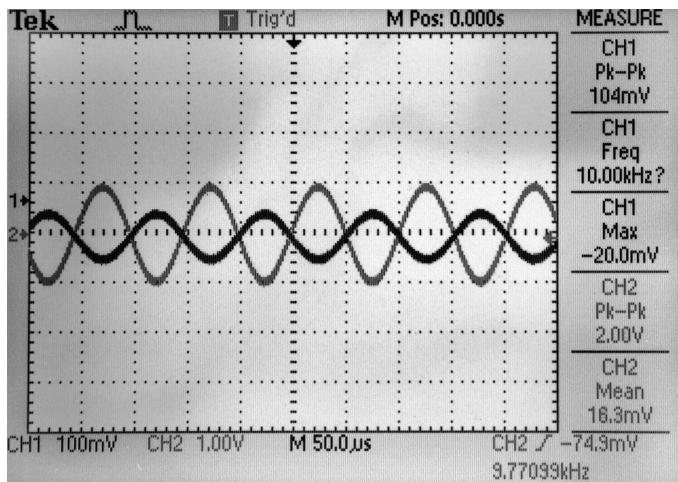**OP.2**

$$V_{out} = 2.0 \text{ V} \quad (\text{Pk-Pk})$$

$$V_{in} (\text{CH1}) \\ V_{out} (\text{CH2})$$



## Commentary

- The DC operating point analysis results yielded inconclusive results compared to the calculated results. However, we see from figure OP.1 that the output signal is yielding increased gain and the correct phase shift. Although the resulting measured values do not appear reasonably close at all, at least the output waveform positively correlates with that of the calculated waveforms. From figure OP.2 which was achieved from another lab colleague, however, the gain value is a much better match against the calculated values.